

HW5

Saturday, October 12, 2024

12:53 PM


Thiago Gesteira
Thiago Gesteira

Clock							
R0	0	1	0	1	0	0	
R1	0	1	0	0	1	0	
G0	0	0	1	0	1	0	
G1	0	0	0	1	0	1	

The module will have the following IO:


```
input reset, clock;
input R0, R1; // request lines
output G0, G1; // grant lines
```

R0	R1	G0	G1
0	0	0	0
1	1	1	0
0	0	0	1
1	0	1	0
0	1	0	1

 

R0 R1


No FSM design

 


States:

G0 G1

input:
R0 R1

 

 

inputs
R0, R1

out
G0, G1

test fixture

// Code your design here

module simpleArbiter (

input clk,

input rst,

input r0,

input r1,

output reg g0,

output reg g1

);

parameter [1:0] S0 = 2'b00;

parameter [1:0] S1 = 2'b01;

parameter [1:0] S2 = 2'b10;

parameter [1:0] S3 = 2'b11;

reg [1:0] state, next_state;

always @ (rst) begin

design

```

        state <= S0;
    end

    always @(*) begin
    reg [1:0] in;
    in = {r0,r1};

        g0 = 0;
        g1 = 0;

        case (state)
            S0: begin
                case (in)
                    2'b00: next_state <= S0;
                    2'b01: next_state <= S2;
                    2'b10: next_state <= S1;
                    2'b11: next_state <= S3;
                endcase
            end
            S1: begin
                g0 = 1;
                next_state <= S0;
            end
            S2: begin
                g1 = 1;
                next_state <= S0;
            end
            S3: begin
                g0 = 1;
                next_state <= S2;
            end
        endcase
    end

    always @(posedge clk) begin
        state <= next_state;
    end

```

```
endmodule
```

```
`timescale 1ns/1ps
```

```
module simpleArbiter_tb;
```

```
    // Testbench signals
```

```
    reg clk;
```

```
    reg rst;
```

```
    reg r0;
```

```
    reg r1;
```

```
    wire g0;
```

```
    wire g1;
```

```
    // Instantiate the simpleArbiter module
```

```
    simpleArbiter uut (
```

```
        .clk(clk),
```

```
        .rst(rst),
```

```
        .r0(r0),
```

```
        .r1(r1),
```

```
        .g0(g0),
```

```
        .g1(g1)
```

```
    );
```

```
    // Clock generation: 10ns period (100MHz)
```

```
    initial begin
```

```
        clk = 0;
```

```
        forever #5 clk = ~clk; // Toggle every 5ns
```

```
    end
```

```
    // Test sequence
```

```
    initial begin
```

```
        // Dumping waveform for EDA Playground
```

```
        $dumpfile("simpleArbiter_tb.vcd");
```

```
        $dumpvars(0, simpleArbiter_tb);
```

```
        // Initialize inputs
```

```
        rst = 1;
```

```

r0 = 0;
r1 = 0;

// Apply reset for a few cycles
#10 rst = 0;
#10 rst = 1;

// Start test cases

// Test case 1: No requests
#20 r0 = 0; r1 = 0; // No request (idle state)
#20;

// Test case 2: Only R0 requests
#20 r0 = 1; r1 = 0; // R0 requests
#20 r0 = 0; // Clear R0 request
#20;

// Test case 3: Only R1 requests
#20 r0 = 0; r1 = 1; // R1 requests
#20 r1 = 0; // Clear R1 request
#20;


// Test case 4: Both R0 and R1 request at the same time
#20 r0 = 1; r1 = 1; // Both requests
#20 r0 = 0; r1 = 0; // Clear both requests
#20;

// Test case 5: R0 and R1 alternate requests
#20 r0 = 1; r1 = 0; // R0 requests
#20 r0 = 0; r1 = 1; // R1 requests
#20 r0 = 1; r1 = 1; // Both request
#20 r0 = 0; r1 = 0; // Clear both
#20;

// End of simulation
#50 $finish;
end

```

endmodule

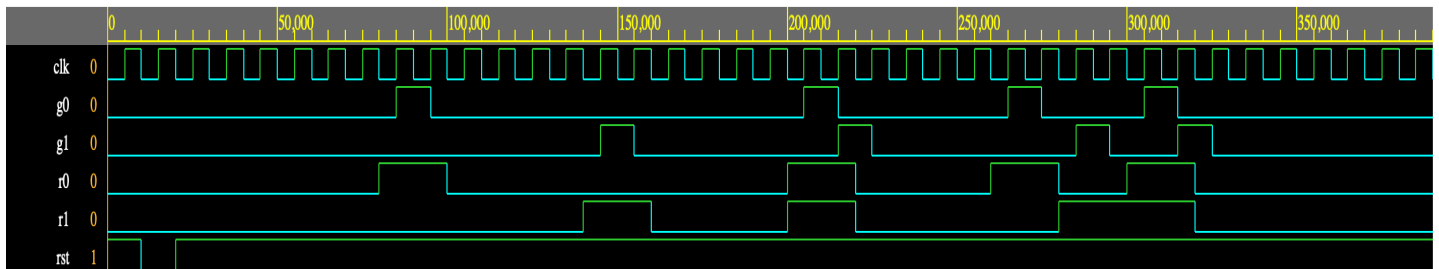

Slack (setup path): 0.15 ns

Slack (hold path): 0.05 ns

Total cell area: 3456.78

Combinational area: 1200.45

Sequential area: 2256.33