

3. Verilog I

Dr. Paul D. Franzon

Units within this module:

1. Introduction HDL-based Design with Verilog
2. A complete example: count.v
Design
3. A complete example: count.v
Verification → Synthesis
4. Further examples

3.1 Introduction to Design With Verilog

Dr. Paul D. Franzon

Outline

1. HDL-based Design Flow
2. Introduction to the Verilog Hardware Description Language
3. Main features used in synthesizable design

References

1. Quick Reference Guides
2. Ciletti, Ch. 4, Appendix I.
3. Smith & Franzon, Chapter 2-6

Attachments Required : Standard Synthesis Script (count.dc)

See Course Outline for further list of references

Course “Mantras”

- One clock, one edge, Flip-flops only
- Design BEFORE coding
- Behavior implies function
- Clearly separate control and datapath



Objectives

- Describe the THREE coding styles that make up RTL
- Describe basic contrasts of VHDL to Verilog
- Describe the basic structure of a Verilog Module

Motivation

- Starting to get into core of this course
 - How to design using HDLs
- The complexity is NOT in the language but how to use it
 - Design before coding
 - ◆ Each design portion becomes a portion of code
 - Behavior implies function
 - ◆ Expected behavior of a piece of HDL must match behavior of corresponding logic

References

- Sutherland Quick Reference Guide
- Ciletti:
 - Sections 5.1 – 5.9 : Go into more detail than I do (for now)
- Smith & Franzon:
 - Section 6.4 : teaches these basic constructs

Detailed Outline

1. Purpose of HDLs
2. Describing flip-flops
3. Structure of a Verilog Module
4. Verilog vs. VHDL
5. Describing combinational logic

Detailed Outline

1. Purpose of HDLs
2. Describing flip-flops
3. Structure of a Verilog Module
4. Verilog vs. VHDL
5. Describing combinational logic


Purpose of HDLs

- Purpose of Hardware Description Languages:
 - Capture design in Register Transfer Language form
 - ◆ i.e. All registers specified
 - Use to simulate design so as to verify correctness
 - Pass through Synthesis tool to obtain reasonably optimal gate-level design that meets timing
 - Design productivity
 - ◆ Automatic synthesis
 - ◆ Capture design as RTL instead of schematic
 - ◆ Reduces time to create gate level design by an order of magnitude
- Synthesis
 - Basically, a Boolean Combinational Logic optimizer that is timing aware

Basic Verilog Constructs

- Flip-Flop
 - Behavior:
 - ◆ For every positive edge of the clock Q changes to become equal to D
- Write behavior as “code”
 
```
always@(posedge clock)  
  Q <= D;
```



- **always@()**
 - Triggers execution of following code block
 - () called “sensitivity list”
 - ◆ Describes when execution triggered

Mantra #3

- **Behavior implies function**

- Determine the behavior described by the Verilog code
- Choose the hardware with the matching behavior

always@(posedge clock)

Q <= D;



- **Code behavior:**

- Q re-evaluated every time there is a rising edge of the clock
- Q remains unchanged between rising edges

- **This behavior describes the behavior of an edge-triggered Flip-flop**

Verilog example

- What is the behavior and matching logic for this code fragment?


```
always@(clock or D)  
  if (clock) Q <=D;
```

- Hint : always@(foo or bar) triggers execution whenever foo or bar changes

*Q assigned to D whenever clock or D changes and clock=1
Ie. Q tracks D while clock high
Level sensitive latch!*

Flip-Flops

 - Every variable assigned in a block starting with `always@(posedge clock)` or `always@(negedge clock)` becomes the output of an edge-triggered flip-flop
- This is the only way to build flip-flops



Sub-module Summary

- Verilog is used to capture a design at the Register Transfer Level (RTL)
- All variables assigned after an “always@(posedge clock)” statement become the outputs of flip-flops
 - Why? Behavior → Function

Please do sub-module quiz before proceeding to next sub-module

Detailed Outline

1. Purpose of HDLs
2. Describing flip-flops
3. Structure of a Verilog Module
4. Verilog vs. VHDL
5. Describing combinational logic

Verilog Module for Flip-flop

```
module flipflop (D, clock, Q);  
input D, clock;  
output Q;  
reg Q;  
always@(posedge clock)  
begin  
    Q <= D;  
end  
endmodule
```

Module Name
Connected Ports
Port Declarations
Local Variable
Declarations
Code Segments
endmodule

VHDL model for Flip-flop

```
entity flipflop is
    port (clock, D:in bit; Q: out bit);
end flipflop;
architecture test of flipflop is
begin
    process
    begin
        wait until clock'event and clock = `1';
        Q <= D;
    end process;
end test;
```

Verilog vs. VHDL

- Verilog
 - Based on C, originally Cadence proprietary, now an IEEE Standard
 - Quicker to learn, read and design in than VHDL
 - Has more tools supporting its use than VHDL

Verilog vs. VHDL

- VHDL

- VHSIC (Very High Speed Integrated Circuit) Hardware Description Language
- Developed by the Department of Defense, based on ADA
- An IEEE Standard
- More formal than Verilog, e.g. Strong typing
- Has more features than Verilog

Verilog vs. VHDL (cont'd)

- In practice, there is little difference
 - How you design in an HDL is more important than how you code
 - Can shift from one to another in a few days


Detailed Outline

1. Purpose of HDLs
2. Describing flip-flops
3. Structure of a Verilog Module
4. Verilog vs. VHDL
5. Describing combinational logic

Verilog Combinational Logic

- Combinational Logic Example
- How would you describe the behavior of this function in words?

 *If $a=1$, then $foo = b \text{ xor } c$,
else $foo = b \text{ or } c$*



- And in Code?

```
always@(a or b or c)
if (a) foo = b ^ c;
else foo = b | c;
```


*foo can change when any of
a,b or c changes SO code must
be rerun whenever any of these
Change.*

Behavior → Function

always@(a or b or c)

if (a) foo = b^c;

else foo = b | c;

 

- All logical inputs in sensitivity list
- If; else → Multiplexor
- Behavior = whenever input changes, foo = mux of XOR or OR
- Same behavior as combinational logic


Procedural Blocks

- Statement block starting with an “always@” statement is called a procedural block
- Why?
 - Statements in block are generally executed in sequence (i.e. procedurally)

Alternative Coding Style for CL

- Verilog has a short hand way to capture combinational logic
- Called “continuous assignment”

```
assign foo = a ? b^c : b | c;
```

 


LHS re-evaluated whenever anything in RHS changes

```
f = a ? d : e; same as “if (a) f=d else f=e;
```

Input Logic to Flip-Flops

- Can include **some** combinational logic in FF procedural block
 
```
always@(posedge clock)
  if (a) foo <= c;
  else foo <= b;
```



- Behavior → function
 - foo is re-evaluated on every clock edge → output of FF
 - If;else → MUX
- Best to limit this practice to simple case statements and if-else statements (will explain why in a later module)

RTL Coding Styles

- That's it!
- Three coding styles
 - **always@(???edge clock)** → FFs and input logic
 - **always@(*)** → Combinational logic (CL) specified by its behavior
 - **assign a =** → Continuous Assignment CL specified as structure
- The hard part is NOT coding but DESIGN

Summary Exercise

What does each piece of logic specify?

Flip Flops and Associated Input Logic

```
always@(posedge clock)
  case (sel)
    0 : E <= D + B;
    1 : E <= B;
  endcase
```

Simple Combinational Logic

```
assign H = C | F;
```

Complex Combinational Logic

```
always@(A or B or C)
  case (A)
    2'b00 : D = B;
    2'b01 : D = C;
    2'b10 : D = 1'b0;
    2'b11 : D = 1'b1;
  endcase
```

Summary

- Three basic synthesizable VL styles
 - `always@(posedge clock)` → Flip-flops
 - `always@(*)` → Combinational logic specified as behavior
 - `assign` → Combinational logic specified as structure

Please do the sub-module quiz before proceeding to the first Verilog 1.2 sub-module