

3. Verilog I

Dr. Paul D. Franzon

Major units within this module

1. Introduction HDL-based Design with Verilog
2. A complete example: count.v
Design
3. A complete example: count.v
Verification → Synthesis
4. Further examples

3.2 *A complete example: count.v*

Dr. Paul D. Franzon

Outline

1. Design before coding
2. count.v example
3. How verilog works internally

References

1. Quick Reference Guides
2. Ciletti, Ch. 4, Appendix I.
3. Smith & Franzon, Chapter 2-6

Attachments Required : Standard Synthesis Script (count.dc)

See Course Outline for further list of references

Objectives and Motivation

Objectives:

- Understand how to execute the mantra “Always Design Before Coding”.
- Understand how Verilog models the intrinsic parallelism of hardware.

Motivation:

- “put it all together” in big picture
- Start understanding how HDL models intrinsic parallelism of hardware
UNLIKE C
 - Useful to understand basics of “what is under the hood”

References

- Sutherland quick reference guide : Summary of main statement types
<http://www.sutherland-hdl.com/reference-guides.php>
- Tutorial 1: Goes through tool usage with this example
- Ciletti:
 - Section 4.1 : Basic Verilog Structures
 - Appendices: A-I : Verilog features
- Smith and Franzon:
 - Section 6.5 : Follows this example

Outline

1. Design before coding
2. Steps in design
3. Counter Example – Verilog 95
4. Counter Example – other coding styles
4. Counter Example – Verilog 2001
6. How Verilog operates internally

Outline

1. Design before coding
2. Steps in design
3. Counter Example – Verilog 95
4. Counter Example – other coding styles
5. Counter Example – Verilog 2001
6. How Verilog operates internally

Mantra #2

- The most important one for this course

ALWAYS DESIGN BEFORE CODING

- Why?
 - Must code at Register Transfer Level
 - ➔ Registers and “transfer” (combinational) logic must be worked out before coding can start



Design Before Coding

- Automatic synthesis does NOT relieve you of logic design
- It does relieve you of:
 - Logic optimization
 - Timing calculations and control
 - In many cases, detailed logic design
- If you don't DESIGN BEFORE CODING, you are likely to end up with the following:
 - A very slow clock (long critical path)
 - Poor performance and large area
 - Non-synthesizable Verilog
 - Many HDL lint errors



Avoid Temptation!

- Temptation #1:
 - “Verilog looks like C, so I’ll write the algorithm in C and turn it into Verilog with a few always@ statements”
- Usual results:
 - Synthesis problems, unknown clock level timing, too many registers

Avoid Temptation! (cont'd)

- Temptation #2
 - “I can’t work out how to design it, so I’ll code up something that looks right and let Synthesis fix it”
- Usual result
 - Synthesis DOES NOT fix it

Avoid Temptation! (cont'd)

- Temptation #3
 - “Look at these neat coding structures available in Verilog, I’ll write more elegant code and get better results”
- Usual result of temptation #3
 - Neophytes : Synthesis problems
 - Experts: Works fine but does not usually give a smaller or faster design + makes code harder to read and maintain
- A better logic structure, not better code gives a better design

Outline

1. Design before coding
2. Steps in design
3. Counter Example – Verilog 95
4. Counter Example – other coding styles
5. Counter Example – Verilog 2001
6. How Verilog operates internally

Design Before Coding


Steps in Design

1. Work out the hardware algorithm and overall strategy
2. Identify and name all the registers (flip-flops)
 - Determine system timing while doing this
3. Identify the behavior of each “cloud” of combinational logic
4. TRANSLATE design to RTL
5. Verify Design
6. Synthesize Design

Design Example: Count Down Timer

- Specification:

 - 4-bit counter
- count value loaded from `in` on a positive clock edge when `latch` is high, latch has priority.
- count value decremented by 1 on a positive clock edge while `dec` is high.
- decrement stops at 0
- `zero` flag active high whenever count value is 0



What NOT To Do

- Coding before design:

```
always@(posedge clock)
for (value=in;value>=0;value--)
  if (value==0) zero = 1
  else zero = 0;
```

- OR:

```
always@(posedge clock)
for (value=in;value>=0;value--)
  @(posedge clock)
  if (value==0) zero = 1
  else zero = 0;
```


Strategy

1. Work out the hardware algorithm and overall strategy

- Strategy:
 - Load 'in' into a register
 - Decrement value of register while 'dec' high
 - Monitor register values to determine when zero


Design

 2. Identify and name all the registers (flip-flops)



Design (cont'd)

 3. Identify the behavior of each “cloud” of combinational logic



4. TRANSLATE design to RTL

```
module counter (clock, in, latch, dec, zero);

input          clock;    /* clock */
input [3:0] in;         /* starting count */
input          latch;    /* latch `in' when high */
input          dec;      /* decrement count when dec high */
output         zero;     /* high when count down to zero */

reg [3:0] value;    /* current count value */
wire      zero;

always@(posedge clock)
begin
    if (latch) value <= in;
    else if (dec && !zero) value <= value - 1'b1;
end

assign zero = (value == 4'b0);
endmodule /* counter */
```

Features in Verilog Code

Note that it follows the hardware design, not the 'C' specification

Multibit variables:

```
reg [3:0] value;
```

4-bit 'signal' [MSB:LSB] i.e. *value[3] value[2] ... value[0]*

**BIG
ENDIAN**

Specifying constant values:

```
1'b1;           4'b0;
```

size 'base value; size = # bits, HERE: base = binary
NOTE: zero filled to left

Procedural Block:

```
always@(          ) Executes whenever variables in sensitivity list (   ) change value
  begin           change as indicated
    ↓
  end             Usually statements execute in sequence, i.e. procedurally
                  begin ... end only needed if more than one statement in block
```

Design Example ... Verilog

- Continuous Assignment:

`assign` is used to implement combinational logic directly

Questions

1. When is the procedural block following the `always@(posedge clock)` executed?
Whenever clock 0 -> 1


2. When is 'zero' evaluated?
Whenever any variable on the RHS changes.

3. How is a comment done?
// or / ... */*

4. What does `1'b1` mean?
1-bit constant, value 1

5. What does `reg [3:0] value;` declare?
4-bit variable, procedurally assigned.

Behavior → Function

 

```
always@(posedge clock)
begin
    if (latch) value = in;
    else if (dec && !zero) value = value - 1'b1;
end
```

```
assign zero = (value == 1'b0);
```

Sub-module Summary

- Design BEFORE coding
- After design
 - Registers + input mux → always@(posedge clock) if-else or case
 - Combinational logic → assign or always@(*) procedural block

Proceed to quiz and onto next sub-module

Outline

1. Design before coding
2. Steps in design
3. Counter Example – Verilog 95
4. Counter Example – other coding styles
5. Counter Example – Verilog 2001
6. How Verilog operates internally

Misc. Alternative Coding

```

module counter ( clock, in, latch, dec, zero);
  // Simple down counter with zero flag
  input          clock;    /* clock */
  input [3:0]     in;       /* starting count */
  input          latch;    /* latch `in' when high */
  input          dec;      /* decrement count when dec high */
  output         zero;     /* high when count down to zero */

  reg [3:0]      value;    /* current count value */
  wire          zero;
  wire [3:0]     value_minus1;
  reg [3:0]      mux_out;

  // Count Flip-flops with input multiplexor
  always@(posedge clock)begin
    value <= mux_out;
  end

  always @(*) begin
    if(latch) begin
      mux_out <= in;
    end
    else if(dec && !zero) begin
      mux_out <= value_minus1;
    end
    else begin
      mux_out <= value;
    end
  end
  assign value_minus1 = value - 1'b1;
  // combinational logic for zero flag
  assign zero = ~|value;
endmodule /* counter */

```

“Simplified” style

*- Clearly separates comb. Logic
from FFs*

- Use if you get confused

Alternative Coding

```

module counter ( clock, in, latch, dec, zero);
  // Simple down counter with zero flag
  input          clock;    /* clock */
  input [3:0]     in;       /* starting count */
  input          latch;    /* latch 'in' when high */
  input          dec;      /* decrement count when dec high */
  output         zero;     /* high when count down to zero */

  reg [3:0] value; /* current count value */
  reg      zero;
  // register 'value' and associated input logic
  always@(posedge clock) begin
    if (latch) value <= in;
    else if (dec && !zero) value <= value - 1'b1;
  end
  // combinational logic to produce 'zero' flag
  always@(value) begin
    if(value == 4'b0)
      zero = 1'b1;
    else
      zero = 1'b0;
  end
endmodule /* counter */

```

Outline

1. Design before coding
2. Steps in design
3. Counter Example – Verilog 95
4. Counter Example – other coding styles
4. Counter Example – Verilog 2001
6. How Verilog operates internally

Verilog 2001 Version

```

module counter (      input      clock, Combine Port List;
                     input      in,      Port Declarations;
                     input      latch,    and Variable Declarations
                     input      dec,
                     output      reg      zero);

/* current count value */
reg [3:0] value;

always@(posedge clock) begin
    if (latch)
        value <= in;
    else if (dec && !zero)
        value <= value - 1'b1;
end

always@(*) begin
    if(value == 4'b0)
        zero = 1;
    else
        zero = 0;
end
endmodule /* counter */

```

*Automatic sensitivity list
(ONLY for combinational
logic)*

Sub-module Summary

- Different coding styles:
 - Combining mux input with register in one block
 - Clearly separating registers and all combinational logic
 - Simple logic can be expressed either in a procedural block or in an assign statement
 - ◆ Assign limited to ONE line
 - Synthesis results do not depend on coding style
- Verilog 2001
 - Improves coding efficiency
 - ◆ Combining ports and declarations
 - ◆ always@(*)
 - I recommend just using this style


Please proceed to quiz and next sub-module

Outline

 1. Design before coding
2. Steps in design
3. Counter Example – Verilog 95
4. Counter Example – other coding styles
4. Counter Example – Verilog 2001
6. How Verilog operates internally

Intrinsic Parallelism

- How Verilog models the intrinsic parallelism of hardware



Want the appearance that F and G change at the same time – How?

Intrinsic Paralellism

- Algorithm for
always@(A) G = |A;
assign F = E ^ A;



*Simulation
time is "frozen
during
evaluation*

when A changes:

In same time "step" the following steps
are performed internally and sequentially:

nextG = |A;

nextF = E ^ A;

At end of time step:

G = nextG; F=nextF;


*In waveform viewer
see G and F changing
simultaneously*

*"Hidden" internal variables
used for sequential evaluation*

Actual variables are assigned once all known

Timing

 - The RTL only specifies the clock level timing, logic has zero delay
- The internal logic delays are worked out (and optimized) during synthesis
- Pre-synthesis, many signals will look like they are changing right on each clock edge
 - Think of them changing just after the clock edge



Sub-module Summary

- Verilog operates as follows:
 - Statement and block triggers are stored
 - ◆ E.g. always@ contents and RHS of assign's
 - When a set of statements and blocks are triggered time is frozen while they are all evaluated
 - ◆ Internal variables are used during this evaluation
 - ◆ Visible variables are updated at the end of the evaluation
 - ◆ This happens in one instant of simulation time, as it appears on the screen

Proceed to the quiz and next unit